

OHM'S LAW

A Self-Study Tutorial

$$V = I \times R$$

Voltage • Current • Resistance

Calculate any one quantity when you know the other two

Name: _____

Date: _____

Section 1: What Is Ohm's Law?

Ohm's Law is one of the most important and widely used principles in electricity. It describes the relationship between three key quantities in any electrical circuit:

Quantity	Symbol / Unit	What it means
Voltage	V (volts)	The electrical 'push' or pressure that drives current around a circuit
Current	I (amperes)	The flow of electric charge — how much electricity moves per second
Resistance	R (ohms, Ω)	The opposition to current flow — how hard the circuit resists the push

Ohm's Law — The Core Statement

The voltage across a conductor is directly proportional to the current flowing through it, provided temperature remains constant. Written as a formula: $V = I \times R$

In plain English: if you double the voltage and keep resistance the same, the current doubles. If you double the resistance and keep voltage the same, the current halves.


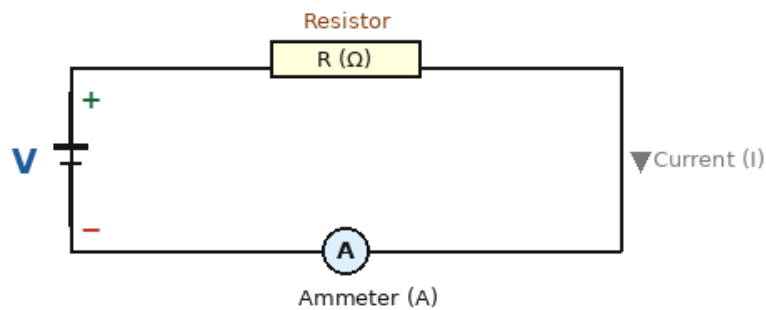


Figure 1: A basic series circuit showing V, I and R

Section 2: The Ohm's Law Triangle

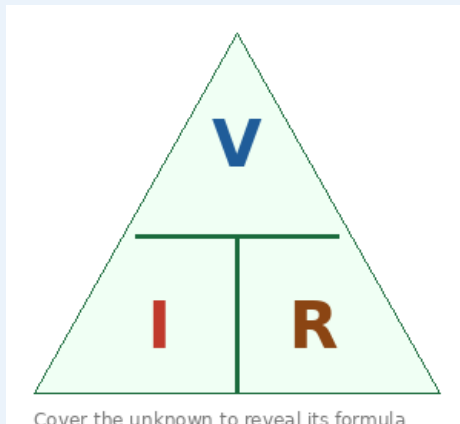The Ohm's Law triangle is a simple tool that lets you instantly see which formula to use, depending on which quantity you need to find.



Cover the unknown to reveal its formula

Figure 2: The Ohm's Law triangle

How to use the triangle

1. Find the letter you want to calculate.
2. Cover it with your finger.
3. What remains shows you the formula:

Cover	Formula revealed
V	$V = I \times R$
I	$I = V \div R$
R	$R = V \div I$

The Three Formulae — at a glance

$V = I \times R$ (to find Voltage) $I = V \div R$ (to find Current) $R = V \div I$ (to find Resistance)

Section 3: Calculating Each Quantity — Step by Step

3.1 Calculating Voltage ($V = I \times R$)

Use when: you know the current (I) and the resistance (R) and need to find the voltage (V).

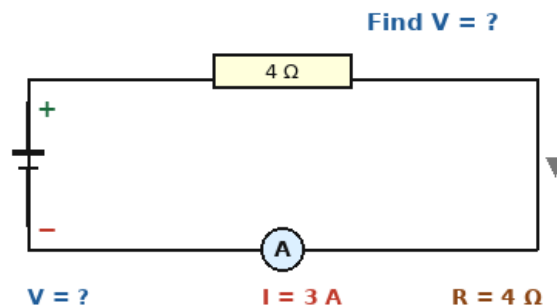


Figure 3: Find the voltage across a 4Ω resistor with 3 A flowing through it

Worked Example — Finding Voltage

A resistor of 4Ω has a current of 3 A flowing through it. What is the voltage across the resistor?

1. Write down what you know: $I = 3 \text{ A}$, $R = 4 \Omega$
2. Choose the correct formula: $V = I \times R$
3. Substitute the values: $V = 3 \times 4 = \mathbf{12 \text{ V}}$
4. State the answer with its unit: The voltage is 12 volts.

Check your answer

Does it make sense? Larger current or larger resistance should give a larger voltage. Here, both values are moderate, and 12 V is a reasonable result (a typical car battery is 12 V).

3.2 Calculating Current ($I = V \div R$)

Use when: you know the voltage (V) and the resistance (R) and need to find the current (I).

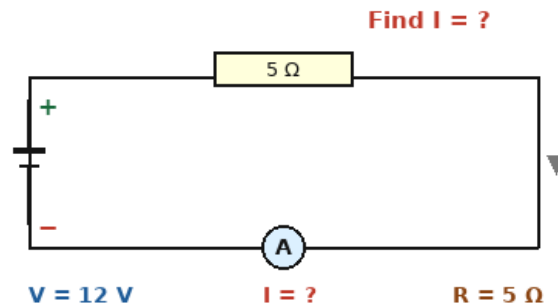


Figure 4: Find the current through a $5\ \Omega$ resistor connected to a 12 V supply

Worked Example — Finding Current

A 12 V battery is connected to a $5\ \Omega$ resistor. What current flows in the circuit?

1. Write down what you know: $V = 12\ \text{V}$, $R = 5\ \Omega$
2. Choose the correct formula: $I = V \div R$
3. Substitute the values: $I = 12 \div 5 = \mathbf{2.4\ \text{A}}$
4. State the answer with its unit: The current is 2.4 amperes.

Check your answer

A 12 V source pushing through $5\ \Omega$ should give a moderate current — 2.4 A is reasonable. If resistance were doubled to $10\ \Omega$, current would halve to 1.2 A.

3.3 Calculating Resistance ($R = V \div I$)

Use when: you know the voltage (V) and the current (I) and need to find the resistance (R).

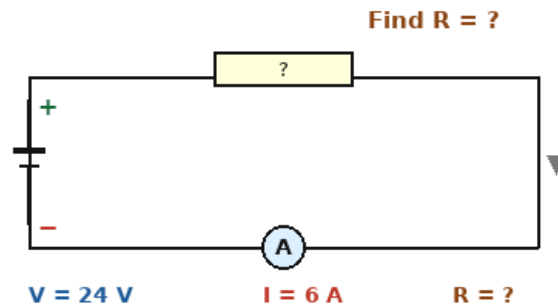


Figure 5: Find the resistance in a circuit with 24 V supply and 6 A current

Worked Example — Finding Resistance

A circuit has a 24 V power supply and a current of 6 A flows. What is the resistance?

1. Write down what you know: $V = 24\text{ V}$, $I = 6\text{ A}$
2. Choose the correct formula: $R = V \div I$
3. Substitute the values: $R = 24 \div 6 = 4\ \Omega$
4. State the answer with its unit: The resistance is 4 ohms.

The Four-Step Method — use it every time

Step 1: Write down the known values with units. **Step 2:** Select the correct formula from the triangle. **Step 3:** Substitute numbers into the formula and calculate. **Step 4:** Write the answer with its correct unit (V, A, or Ω).

Section 4: Activities

Activity 1: Name the Formula

For each circuit, state which formula you would use and circle the quantity you are finding.

Known values	Find...	Formula to use
$V = 20\text{ V}, R = 4\ \Omega$	$I = ?$	
$I = 5\text{ A}, R = 6\ \Omega$	$V = ?$	
$V = 15\text{ V}, I = 3\text{ A}$	$R = ?$	
$V = 9\text{ V}, R = 3\ \Omega$	$I = ?$	
$I = 2\text{ A}, R = 10\ \Omega$	$V = ?$	

Activity 2: Calculate and Show Your Working

Use the four-step method for each question. Show all working clearly.

Question 1 — Find the Voltage

A resistor of $8\ \Omega$ has a current of 2 A flowing through it. Calculate the voltage.

Step 1 — Known values:

Step 2 — Formula:

Step 3 — Calculation:

Step 4 — Answer:

Question 2 — Find the Current

A 30 V supply is connected across a 6 Ω resistor. Calculate the current.

Step 1 — Known values:

Step 2 — Formula:

Step 3 — Calculation:

Step 4 — Answer:

Question 3 — Find the Resistance

A current of 4 A flows when a voltage of 20 V is applied. Find the resistance.

Step 1 — Known values:

Step 2 — Formula:

Step 3 — Calculation:

Step 4 — Answer:

Activity 3: Real-World Scenarios

Scenario 1 — The Torch Bulb

A torch bulb has a resistance of 10 Ω . It is connected to a 6 V battery.

Question: What current flows through the bulb?

Working:

Answer: _____

Scenario 2 — The Electric Heater

An electric heater draws a current of 5 A from a 230 V mains supply.

Question: What is the resistance of the heater element?

Working:

Answer: _____

Scenario 3 — The Car Battery

A car starter motor has a resistance of $0.5\ \Omega$ and draws a current of 24 A.

Question: What voltage does the battery supply to the starter motor?

Working:

Answer: _____

Activity 4: Sketch the Circuit

For each question below, draw a simple circuit sketch in the box provided, label the known values, and calculate the missing quantity.

Problem A: $V = 18\text{ V}$, $R = 9\ \Omega$. Find I .	Problem B: $I = 3\text{ A}$, $R = 7\ \Omega$. Find V .
Circuit sketch: <hr/>	Circuit sketch: <hr/>
Answer: _____	Answer: _____

Activity 5: True or False?

Circle TRUE or FALSE. Write a correction on the line if the statement is false.

1. If voltage is doubled and resistance stays the same, current doubles. TRUE / FALSE

Correction: _____

2. The formula for finding resistance is $R = I \times V$. TRUE / FALSE

Correction: _____

3. Ohm's Law applies when temperature is kept constant. TRUE / FALSE

Correction: _____

4. In the triangle, covering V reveals $I \times R$. TRUE / FALSE

Correction: _____

Section 5: Self-Check Quiz

Instructions

Answer all questions without referring to earlier sections. When finished, turn to Section 6 for the answer key. Award yourself the points shown for each correct answer.

Part A: Multiple Choice (1 point each)

1. Ohm's Law states that $V =$:

- a) a) $V + R$
- b) b) $I \times R$
- c) c) $I \div R$
- d) d) $R \div I$

2. A circuit has $V = 10 \text{ V}$ and $R = 2 \Omega$. The current is:

- a) a) 20 A
- b) b) 0.2 A
- c) c) 5 A
- d) d) 8 A

3. The unit of resistance is the:

- a) a) volt
- b) b) ampere
- c) c) watt
- d) d) ohm

4. In the Ohm's Law triangle, covering I reveals:

- a) a) $V \div R$
- b) b) $V \times R$
- c) c) $R \div V$
- d) d) $V + R$

5. If resistance doubles and voltage stays the same, the current:

- a) a) doubles
- b) b) stays the same
- c) c) halves
- d) d) becomes zero

Part B: Short Answer (2 points each)

6. A 9 V battery is connected to a 3 Ω resistor. Calculate the current.

Working: _____ Answer: _____

7. A current of 2 A flows through a 7 Ω resistor. What is the voltage?

Working: _____ Answer: _____

8. A 12 V circuit has a current of 4 A. What is the resistance?

Working: _____ Answer: _____

9. Write the three rearrangements of Ohm's Law.

V = _____ I = _____ R = _____

10. State Ohm's Law in one sentence (no formula).

My Score: _____ / 15

Section 6: Answer Key

For Students

Only turn to this page after completing the quiz. Reviewing your mistakes is the most valuable part of self-study!

Activity 1: Name the Formula — Answers

Known values	Find	Formula
$V=20\text{ V}, R=4\ \Omega$	I	$I = V \div R = 5\text{ A}$
$I=5\text{ A}, R=6\ \Omega$	V	$V = I \times R = 30\text{ V}$
$V=15\text{ V}, I=3\text{ A}$	R	$R = V \div I = 5\ \Omega$
$V=9\text{ V}, R=3\ \Omega$	I	$I = V \div R = 3\text{ A}$
$I=2\text{ A}, R=10\ \Omega$	V	$V = I \times R = 20\text{ V}$

Activity 2: Calculate and Show Your Working — Answers

Q1 — Voltage

$$V = I \times R = 2 \times 8 = 16\text{ V}$$

Q2 — Current

$$I = V \div R = 30 \div 6 = 5\text{ A}$$

Q3 — Resistance

$$R = V \div I = 20 \div 4 = 5\ \Omega$$

Activity 3: Real-World Scenarios — Answers

Scenario 1

$I = V \div R = 6 \div 10 = 0.6\text{ A}$. A current of 0.6 amperes flows through the bulb.

Scenario 2

$R = V \div I = 230 \div 5 = 46\ \Omega$. The heater element has a resistance of 46 ohms.

Scenario 3

$V = I \times R = 24 \times 0.5 = 12 \text{ V}$. The battery supplies 12 volts to the starter motor.

Activity 5: True or False? — Answers

1. TRUE
2. FALSE — The formula for resistance is $R = V \div I$ (not $V \times I$).
3. TRUE
4. TRUE

Quiz Answer Key

Q	Answer	Q	Answer
1	b) $I \times R$	6	$I = 9 \div 3 = 3 \text{ A}$
2	c) 5 A	7	$V = 2 \times 7 = 14 \text{ V}$
3	d) ohm	8	$R = 12 \div 4 = 3 \Omega$
4	a) $V \div R$	9	$V = I \times R, I = V \div R, R = V \div I$
5	c) halves	10	Voltage = current \times resistance (at constant temp)

Scoring Guide

Score	Level	Next Step
13–15	Excellent!	Move on to series & parallel circuits
9–12	Good — almost there	Review the sections for questions you missed
0–8	Keep practising	Re-read Sections 2 & 3 and redo Activities 2 & 3

Well done for completing this unit! ⚡